

Smart switch cuts transformer turn-on current


ROBERT LINDSEY, HANSVEDT EDM, URBANA, IL

Transformer-core saturation can cause inexplicable fuse blowing, system crashes, or premature switch and relay failure. When a core saturates, it loses its inductive characteristics; primary winding current can then reach extremely high values for several ac cycles. Turning on a transformer may seem fundamental, but in some power-supply designs and control applications, it can be a game of Russian roulette. Because transformers remain polarized when turned off, saturation occurrence is a function of the polarity and phase angle of the ac cycle when you switch the circuit on and off. The smart-switch circuit in **Figure 1** eliminates saturation, improves relay reliability, and provides a tool for determining transformer and relay performance.

The circuit goes beyond typical configurations using zero-crossing or peak-switching relays, by using the polarity of the ac cycle, known phase angles, and soft-starting techniques. **Figure 2** shows that the primary turn-on current of a 220-VA transformer can be disastrous when you use a zero-crossing relay. Trace R1 shows 46A peak with a saturated

core. Trace 1 shows only a few amps with use of the smart-switch circuit. This large difference in current demonstrates the value of the smart switch in controlling transformer magnetization. Switching on during a positive half cycle and off during a negative half cycle or vice versa prevents most core saturation.

Peak switching of the ac voltage during turn-on and -off further reduces the susceptibility to core saturation, regardless of ac polarity. This reduction is an important consideration in the event of an uncontrolled power outage. **Figure 3**, trace R, shows the primary current with peak and same-polarity switching. The vertical scale in **Figures 2** and **3** is 10A per division, and Trace 2 is the relay control voltage. The primary current in **Figure 3** causes some core saturation (note that the current is not bipolar), but the saturation is much lower than that in **Figure 2**. Trace 1 shows the reduced primary current with the use of peak and opposite-polarity switching. Note that transformer designs vary widely; some may favor particular phase angles.

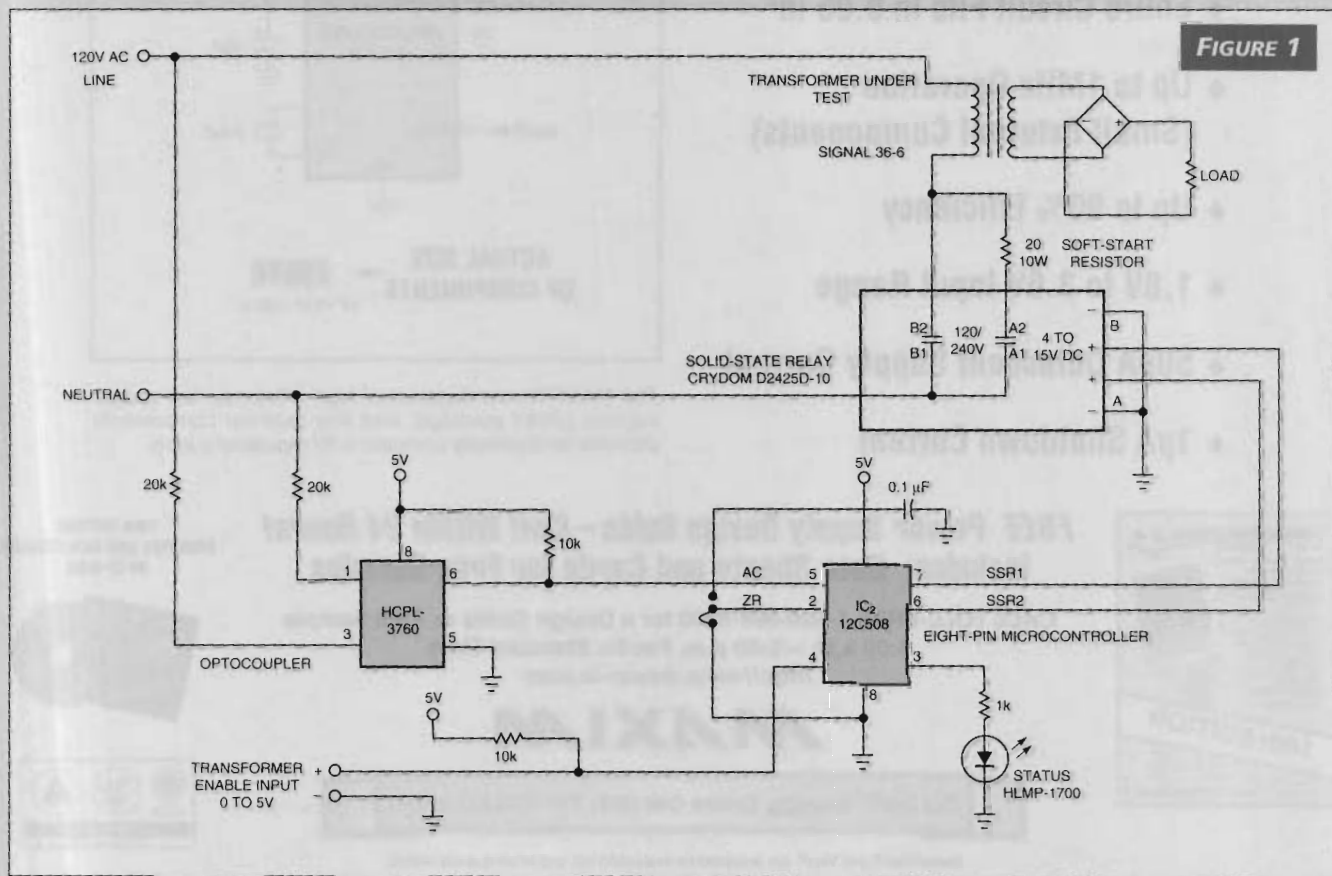**FIGURE 1**

A μ C-controlled smart switch prevents transformer-core saturation, thus averting system crashes and prolonging the life of power-supply relays.

Inrush current from power-supply filter capacitors is also an important design consideration. By using a resistor, an inrush device, or an inductive input filter in the secondary winding, you can reduce this inrush surge. Another solution is to soft-start the transformer by using a resistor in the primary to limit inrush and saturation currents to an acceptable level. After a brief delay, a second solid-state relay shunts the resistor. The Microchip 12C508 μ C uses its internal 4-MHz RC oscillator for all timing. The chip is simple, inexpensive, reliable, and well-suited for this application. For wide temperature variations, you can obtain more accurate

timing by using a 32-kHz crystal. You can download Listing 1, the source code for the μ C's operation, from EDN's Web site www.ednmag.com. At the registered-user area, go into the Software Center to download the file from DI-SIG, #2170.

You can use either zero-crossing or random relays, but the random type works better for transformers. Set Pin 4 high for zero-crossing relays and low for random-turn-on relays. The HCPL-3760 optocoupler determines the polarity and phase of the ac line. The coupler is configured as a near-zero detector. Its output is set to switch on at 50V ac and off at 25V ac.

LISTING 1—SOURCE CODE FOR TRANSFORMER SOLID-STATE-RELAY CONTROLLER

```

; ROBERT LINDSEY
; 1908 KENNY AVE, CHAMPAIGN, IL 61821
; 217 384-5900

; This is a smart switch for controlling a solid state relay that is used
; for controlling the AC primary power to a large transformer. Transformers
; are noted for having extremely high inrush currents due to momentary
; core saturation if the polarization is correct. This version has an optional
; soft start switch that uses a resistor in the primary to limit current
; from the power supply filter capacitors and core saturation. The primary
; function of the code is to always turn the transformer on on the positive
; half of the ac cycle and turn it off on the negative half of the ac cycle.
; Random turn on solid state relays or zero crossing relays can be used.

title "Transformer SSR Controller"
list p-pic12C508, st-off, x-on, n=75, r=dec
include "pic2c508.inc"
CONFIG B'000000001010'

;----- RAM REGISTERS -----
cblock H'0007'
COUNT1 ;test counter
COUNT2 ;test counter
endc

;----- PORT PIN ASSIGNMENTS -----
#define SSR1 GPIO,0 ;pin 7, output, SS relay 1
#define SSR2 GPIO,1 ;pin 6, output, SS relay 2
#define AC GPIO,2 ;pin 5, input, AC polarity, HCPL-3760
#define TE GPIO,3 ;pin 4, input, transformer enable
#define BLEEDER GPIO,4 ;pin 3, output, bleeder resistor
#define ZR GPIO,5 ;pin 2, input, zero crossing or random
;1=Zero crossing, 0=Random turn on

org 0
movlw 0
movwf OSCCAL ;int RC oscillator calibration value

movlw B'10000110' ;wake-up off, pull-ups on, T0 int clk,
option ;T0 prescaler, =128

;----- MAIN -----
bcf SSR1 ;set pin 7 latch low
bcf SSR2 ;set pin 6 latch low
bcf BLEEDER ;set pin 3 latch low

main movlw B'00101100' ;GPIO, 0 - output pin
tris GPIO ;set I/O pin functions

bcf SSR2 ;ssr2 is off
bsf BLEEDER ;bleeder is on
btfss TE ;is TE enable signal high
goto TX0 ;no, so keep checking

movlw 50 ;yes, make sure it was not a glitch
movwf COUNT2
call wait ;wait 50ms
btfss TE ;is TE enable still high
goto TX0 ;no, it was a glitch, keep waiting

bcf BLEEDER ;yes, turn off bleeder resistor
clrf COUNT2 ; 1/4 second delay
call wait ;

movlw 4 ;load COUNT2 with 4ms wait after zero crossing
movwf COUNT2 ;which will be near AC peak
call ACTrig ;wait for +zero crossing of AC voltage
call wait

bsf SSR1 ;turn on SS relay 1 (soft start resistor)
clrf COUNT2 ;load ms counter for 1/4 second delay
call wait ;allow power supply caps to charge

movlw 4 ;load COUNT2 with 4ms wait after zero crossing
movwf COUNT2 ;which will be near AC peak
call ACTrig ;wait for +zero crossing of AC voltage
call wait
bsf SSR2 ;turn on SS relay 2 (main)

;----- TURN OFF -----
; turn off transformer at negative peak

TX1 bcf SSR1 ;ssr1 is on
bsf SSR2 ;ssr2 is on
bcf BLEEDER ;bleeder is off
btfsc TE ;is TE enable signal low
goto TX1 ;no, it is still high, so keep checking

movlw 50 ;yes, make sure it was not a glitch
movwf COUNT2
call wait ;wait 50ms
btfsc TE ;is TE enable still low
goto TX1 ;no, it was a glitch, keep waiting

movlw 12 ;yes, load 12ms wait after zero crossing
btfsc ZR ;using zero crossing SS relay? ZR=1?
movlw 4 ;yes, load 4ms wait after zero crossing
movwf COUNT2 ;which will be near AC peak
call ACTrig ;wait for +zero crossing of AC voltage
call wait
bcf SSR2 ;turn off solid state relay 2
clrf COUNT2 ;1/4 second delay
call wait ;

movlw 12 ;load 12ms wait after zero crossing
btfsc ZR ;using zero crossing SS relay? ZR=1?
movlw 4 ;yes, load 4ms wait after zero crossing

movwf COUNT2 ;which will be near AC peak
call ACTrig ;wait for +zero crossing of AC voltage
call wait
bcf SSR1 ;turn off SS relay 1

clrf COUNT2 ;1/4 second delay
call wait ;

bsf BLEEDER ;turn on bleeder resistor
clrf COUNT2 ;1/4 second delay for power supply bleed down
call wait ;
goto main ;wait for turn-on

;----- AC TRIGGER -----
;wait for a low to high transition from the HCPL-3760 opto-coupler
ACTrig:
acl btfsc AC ;is AC input signal low
goto acl ;no, it is high, keep waiting until low
nop ;yes, it is low now

ac0 btfss AC ;is AC input signal high
goto ac0 ;no, it is low, keep waiting until high
nop ;yes, it is high now
return

;----- MS WAIT DELAY -----
;enter with milli-second value in COUNT2 register
;exits with COUNT1 and COUNT2 = 0

wait:
wait1 clrf COUNT1
wait2 nop
decfsz COUNT1,1
goto wait2
decfsz COUNT2,1
goto wait1
return

end

```



You have the idea. dSPACE has the tool.

For ECU design.

Developing vehicle electronics.

With rapid control prototyping and hardware-in-the-loop simulation - only with one tool.

Speeding-up function development.

With MATLAB/Simulink® and model-based design.

Testing electronic control units.

With the help of complete test benches by dSPACE.

2500 dSPACE systems worldwide:

Audi, BMW, Chrysler, Daewoo,
Delco Electronics, DENSO,
Daimler-Benz, Delphi,
Ferrari, Fiat, Ford,
General Motors,
Honda, Hyundai,
Jaguar, Lucas Varity,
Mazda, Mitsubishi,
Nissan, Peugeot,
Renault, Rover,
Toyota, Volvo.



For more information:

dSPACE GmbH
Technologiepark 25
D-33100 Paderborn
tel.: ++49 5251 1638-0 · fax: ++49 5251 66529
info@dSPACE.de · www.dSPACE.de



dSPACE




CIRCLE NO. 10

EDN


DESIGN IDEAS

FIGURE 2

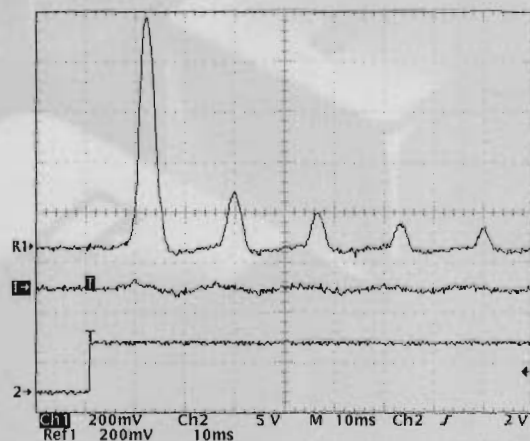

Using only a zero-crossing relay results in core saturation and a disastrous 46A peak current in the transformer's primary winding.

FIGURE 3

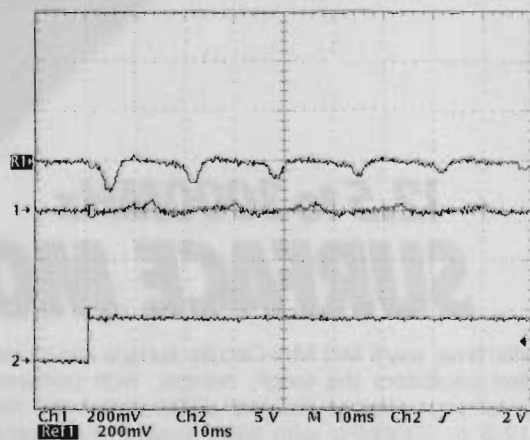

The smart-switch circuit in Figure 1 greatly reduces core saturation, resulting in well-behaved primary current. Trace R1 results from peak and same-polarity switching; trace 1 represents peak and opposite-polarity switching.

One internal diode in the optocoupler rectifies the ac signal to indicate the positive half cycle. The μ C has two solid-state-relay outputs: SSR1 and SSR2. When the Transformer Enable input goes high, the μ C waits 250 msec, detects the next positive edge from the optocoupler, waits 12 msec, and then turns off SSR1. SSR2 has a 250-msec delay from SSR1 and operates as a last-on, first-off output to shunt a soft-start resistor. Pin 3 is an optional output for a power-supply bleed-off switch or a status indicator. (DI #2170)

EDN

To Vote For This Design, Circle No. 371